

HOMEBREW COMPUTER CLUB

NEWSLETTER

Robert Reiling, editor □ Post Office Box 626 □ Mountain View, CA 94042

Volume Number 1, Issue 9

November 30, 1975

TOPICS THIS MONTH

Ray Boaz continues the discussion of multiplexed displays for microcomputer systems. This month he describes a hexadecimal readout that will be of interest to anyone considering the design or modernization of a display.

Up to the minute news is provided by Pete Cornell's coverage of the cassette standard proposed at the recent BYTE symposium. No doubt we will see plenty of discussion about this standard in the immediate future. Pete has the basic data for us in his article.

An original pot position digitizing idea is presented by John Schulein in the Data File section. Try it for converting potentiometer positional data to digital data for your programs.

CLUB MEETING NOVEMBER 12, 1975

Equipment demonstrations at this meeting of 1) TV Dazzler manufactured by CROMEMCO, One First Street, Los Altos, CA 94022, 2) Video Display Module manufactured by Processor Technology Company, 2465 Fourth Street, Berkeley, CA 94710, and 3) IMSAI 8080 System manufactured by IMS Associated Inc., 1922 Republic Avenue, San Leandro, CA 94577. If you missed the demonstrations or don't have complete details on these items you may want to write the manufacturers. Mention that you read about them in the HOMEBREW COMPUTER CLUB NEWSLETTER.

PTC donated a four position expansion board (for an Altair) with four PC card edge connectors to the club to be raffled off. Dan Sokol donated an 8080 CPU IC to the raffle. Two tickets were drawn and the first winner got his pick of the two items (he took the 8080) and the second winner got the expansion board. Tickets were sold for 25¢ apiece and the raffle netted around \$40 which will be used to pay for the newsletter printing and mailing.

Bob Marsh (PTC) spoke of the happenings at the cassette tape standards meeting attended by most of the manufacturers involved with the "home brew" hobbyist computer market. Full coverage of this meeting will be described in an upcoming article in BYTE magazine.

Steve Dompier moderated this meeting in the absence of Lee Felsenstein.

CLUB MEETING NOVEMBER 26, 1975

About 130 people were on hand for this meeting and lots of information was exchanged by the group.

Marty Spergle announced the M&R ENTERPRISES modem Penny Whistle 103 should be available for club members by the end of December. Marty also told us that Tom Pittman is heading the M&R ENTERPRISES' software department. Tom,

(continued on page 6)


INTELLIGENT DISPLAY FOR MICROCOMPUTERS (Continued) - Ray Boaz

Newsletter #8 last month presented the theory of a multiplexed display useful for microcomputer systems with an octal readout of 16 address bits and 8 data bits. This month a hexadecimal readout is described for the same type of microcomputer. The one most interesting point is how similar they are. But, all multiplexed display systems are basically this configuration. The octal circuit presented last month is a "real" circuit, it works as shown. Fine details such as pin numbers, V_{cc} and ground connections, and very important power decoupling was not put on the logic diagram, but this information is all available from the IC Data Sheets. Likewise, this type of information is not included on the hex circuit either. This is not a "construction plan," only a technique of how it really can be done. Oh well, enough of that -- on to the hex circuit.

The same oscillator as in the octal circuit is shown here but likely can be left out since the microcomputer should have a clock that may be used. A 7492 is used on the counter since it has a divide by 6 counter in it. NOTE that the B-C-D outputs are re-labeled A-B-C. The A flip-flop is not used. The relabeled A-B-C are connected to the A-B-C inputs on all the data muxes and the digit decoder. Only six inputs of the data muxes and six outputs of the digit decoder are used since only six digits of display are required for 16 address and 8 data bits in hexadecimal. Here again the counter requires no reset since it divides by six giving states 0-5, the exact requirement. The data muxes are 74151 with only six of the eight inputs used. As shown in Table 1, the mux chart, the number of bits map exactly to the data inputs. No special decoding is required as in the octal circuit. The 7442, one of ten decoders, has input D grounded since it should always be low. Due to the type of segment decoder/driver (D/D) used the digit enable lines must be high and supply current for seven segments. Transistor switches are used to do this. The active low output of the 7442 turns on a transistor which supplies the high level and current required. The pull-up resistor on the digit decoder output lines insure the off transistors are indeed really off. The segment D/D is a Fairchild 9370, which is an active low, open-collector output, hexadecimal decoder/driver able to sink $> 25 \text{ mA}$ output. It decodes hex numbers 0-9, A, b, C, d, E, and F. Since it is active low, it can only drive common anode readouts; therefore, the requirement of the transistor switch discussed earlier. The resistors in series with the segment D/D output lines are used for current limiting and set the brightness of the display. Segment D/D output lines connect to like-segment inputs on each digit, a-a, b-b, ..., f-f, and g-g. The 9370 enable line (E) must be grounded for multiplexed operation. All that's left is the LED readouts. They simply light up as they are turned on by the digit and segment enable lines.

Figure 1 is a comparison between the common cathode type LED digit of the octal circuit and the common anode type LED digit described here. Shown is one output of the 7448 going to one segment of the digit and one open collector output of the 74145. When that segment of that digit is on the current determined by R lights that diode. The 7448 is active high; that is, when the output is high, the LED is forward biased and on; when the output is low, the transistor is a low impedance path to ground and it sinks current away from the LED, thereby keeping it turned off. The common anode circuit shows one 2N5139 digit switch and one 9370 segment output. When that digit and that segment are to be on the 9370 output goes low, the 2N5139 is turned on by the 7442 output going low, and the LED lights up to a brightness determined by the current passed by resistor R.

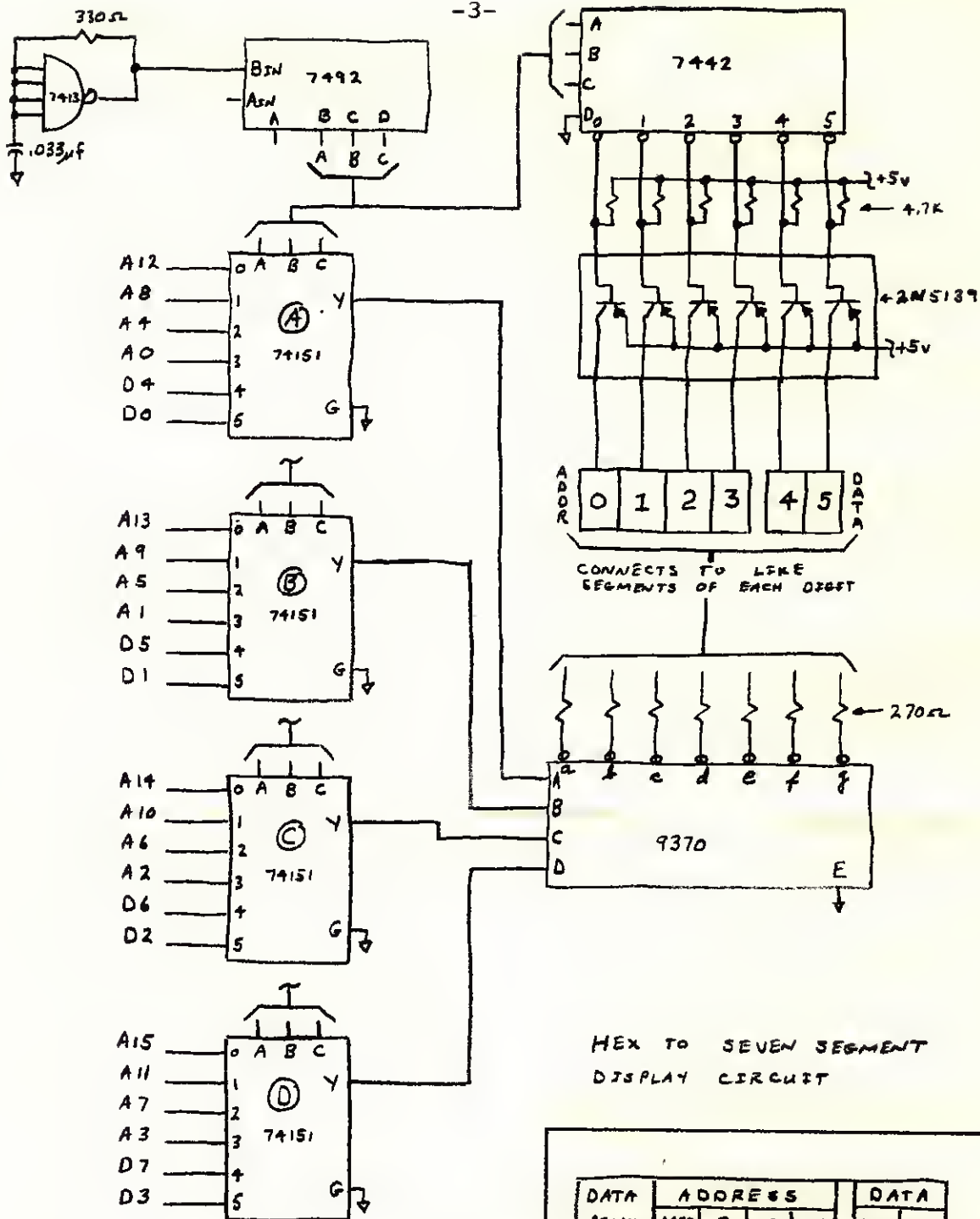
Next month's newsletter will conclude this series on display multiplexing. To be presented then is a switch selectable octal/hex display which requires only nine IC's and nine LED digits.



HEX TO SEVEN SEGMENT
DISPLAY CIRCUIT

DATA MUX	ADDRESS				DATA	
	MSD	2	2	LSB	MSD	LSB
(A)	A12	A8	A4	A0	D4	D0
(B)	A13	A9	A5	A1	D5	D1
(C)	A14	A10	A6	A2	D6	D2
(D)	A15	A11	A7	A3	D7	D3

TABLE 1
HEXADECIMAL MUX CHART

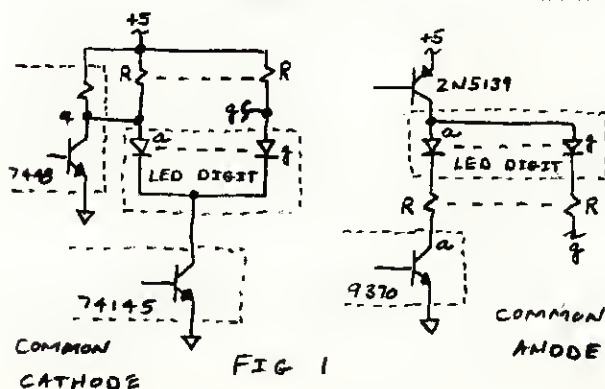

THE NEW CASSETTE INTERFACE PROPOSED AT THE BYTE SYMPOSIUM - Pete Cornell

What follows is a summary of information sent by Harold A. Mauch of Pronetics Corp., Box 28582, Dallas, TX 75228. The source document is available from the club librarian, Gordon French, 325-4209. This is a best effort, but not guaranteed to be error free:

- 1) A Mark (Logic One) is eight cycles of 2400 Hertz.
- 2) A Space (Logic Zero) is four cycles of 1200 Hertz.
- 3) A recorded character will consist of a Space (start) bit, eight data bits, and two or more concluding Mark (stop) bits.
- 4) The eight data bits are organized least significant bit first and concluding with parity if applicable.
- 5) All bits not specifically containing information will be Mark bits (for example: the unused bits when exchanging 5-level coded information).
- 6) The non-information interval between characters will be Mark bits. Variation in the number of fill bits reflects the data rate.

RATIONALE:


Bandwidth: Characteristics of many low cost cassette recorders limit acceptable performance to the 300 - 3000 Hertz range. Outside this range amplitude roll-off and phase shift may be unacceptable.

Modulation: The proposed method is self-clocking and is tolerant of speed variation in excess of $\pm 30\%$, more than adequate for even the cheapest recorders. The constant presence of either 2400 or 1200 Hertz keeps the recorder's AGC circuit happy.

Mark: Since the marking state preconditions the Start bit synchronization, it should be unambiguous with regard to bit cell framing. Selecting the higher of the two modulation frequencies for the Mark state provides this condition.

Redundancy: The redundancy of multiple cycles per bit permits analog or digital integration and the resulting lower error rate in the presence of an adverse environment.

CIRCUIT: Pronetics' schematics are reproduced here without a description of circuit function. It is a touched-up n^{th} generation copy. Hope it reads. They claim that error rates at 300 baud using computer grade tapes are less than one in 10^7 using this circuit. My guess is that substantially similar performance could be had with a simpler and less expensive design. (Why CMOS?) Any input on a better circuit, interface, software or other cassette stuff may be addressed to me, Pete Cornell, Box 714, 94022. Pronetics properly notes that cassette quality has more effect on error performance than recorder quality. Recommended reading: Don Lancaster's Serial Interface article in BYTE #1. I hope this standard catches on. I believe it's good and plan to use it.

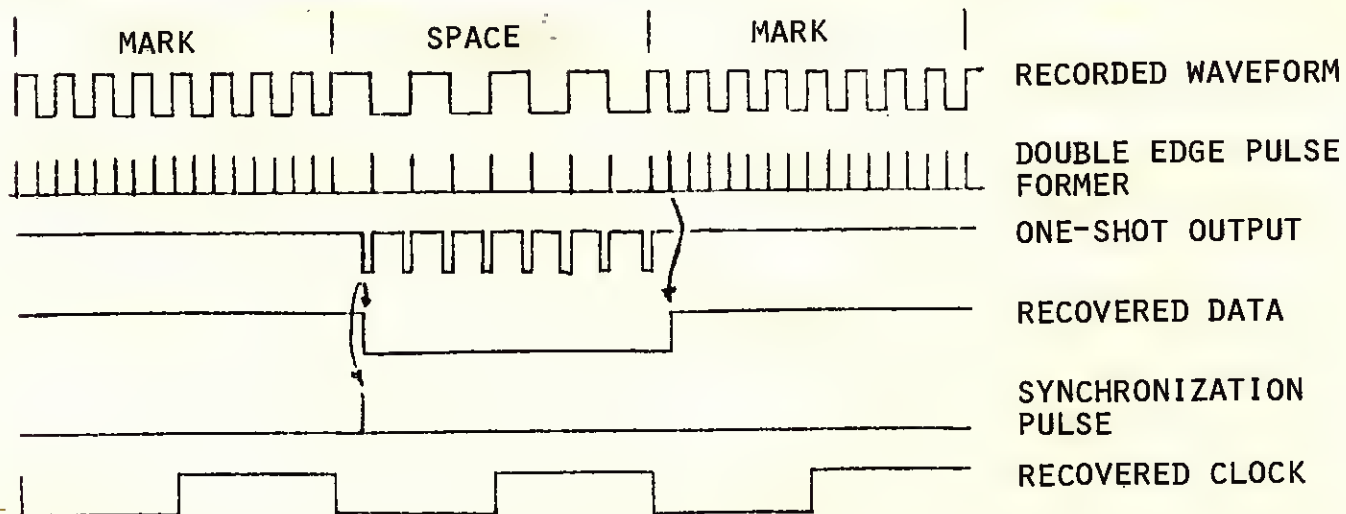

(continued from page 1)

as you may know, maintains the HOMEBREW COMPUTER CLUB NEWSLETTER mailing list on his home computer system.

The TV Dazzler system design has been frozen for several weeks now and the goal for the first shipments is set for December 15th. A club discount will be available if 50 people get together to buy these units. Someone needs to handle this.

Computer stores are opening. The BYTE SHOP, 1061 El Camino Real, Mountain View, CA will open December 8, 1975 with the complete MITS line. Another store (different management) will open in Berkeley but we don't have details.

Gordon French is using the INTEL floating point package on his 8008 system with excellent results.

CALL COMPUTER reports 34 members currently using the K200 account (last months newsletter has details on the K200 account). Also, CALL COMPUTER has a new addition, aDATA GENERAL ECLIPSE C300 with many new capabilities beyond those previously available.

HOLIDAY CLUB MEETING SCHEDULE

The next club meeting is December 10, 1975 at Stanford Linear Accelerator Center, Menlo Park, CA. No club meeting will be held December 24, 1975. Meetings will resume again on January 7, 1976 and follow the regular two week schedule. Meetings begin at 7PM and continue to about 10PM. Ask the guard for directions to the meeting room.

BULLETIN BOARD - Club Members

STAN ROSENFELD - Main interest is in educational use of computers. My first project is to tie into a 360 running APLSV. Need MODEM, EBCDIC adapter, keyboard, and (solenoid?) driver for my IBM non-selectric type-writer. Telephone 255 4076 San Jose - 6570 Dartmoor Wy., San Jose, CA 95129

PLEASE HELP - I'm a student at Foothill High School in Pleasanton. I'm President of a club at our school and I'm interested in trying to form a club in our area, but I can't do it alone. I'm looking for anyone who would be interested in helping me form it. The club would be for anyone interested in computers, electronics, et al. Contact Paul Holbrook, 6104 Crater Lake Ct., Pleasanton, CA 94566 or telephone (415) 462 3816 between 5 - 9PM.

ALTAIR BOARDS - Assembled and working: CPU board \$200; 1K memory board with 256 bytes \$20; FRONT PANEL connected to a MOTHER BOARD and 2 connectors \$125. All boards \$325. Ken McGinnis, Box 2078, San Mateo, CA 94401 Telephone 342 0115.

CONSULTANTS - PATCA, the Professional and Technical Consultants Association is a non-profit association of independent professionals who have joined in a common effort to promote our chosen way of life. We operate a Referral Service (free to potential clients) on behalf of our members. If you would like more information, membership forms etc., telephone PATCA (415) 961 1155, 2680 Bayshore Frontage Rd., Mountain View, CA 94043

EXCHANGE - Seek to exchange newsletters and technical data with organizations or individuals with similar interests. BIT USERS ASSOCIATION, RESOURCE ACCESS CENTER, 3010 4th Ave. South, Minneapolis, Minnesota 55408


POT POSITION DIGITIZING IDEA - John M. Schulein

A scheme to convert the position of a potentiometer arm into a digital value using a cheap commonly available timer IC (NE555) and a few bytes of program in an 8008/8080 μ P system is shown in Figure 1. The software is organized as a subroutine and uses the flags and the A & B registers. The NE555 is triggered by the OUT TRIGGER instruction and then the μ P monitors the output pin of the NE555 in a loop that increments the B register. When the NE555 times out, the program exits from the subroutine and the B register contains a digital representation of the pot position.

The hardware and software shown in Figure 1 was run on an 8008 system with a 2.5 μ s clock and the B register digital output varied from 2 to 65 Hex. The values of the pot and/or the timing capacitor can be modified (see the NE555 data sheet) to suit your processor's speed and the desired range of the digitized output.

Figure 1

Pot Position Digitizing Idea

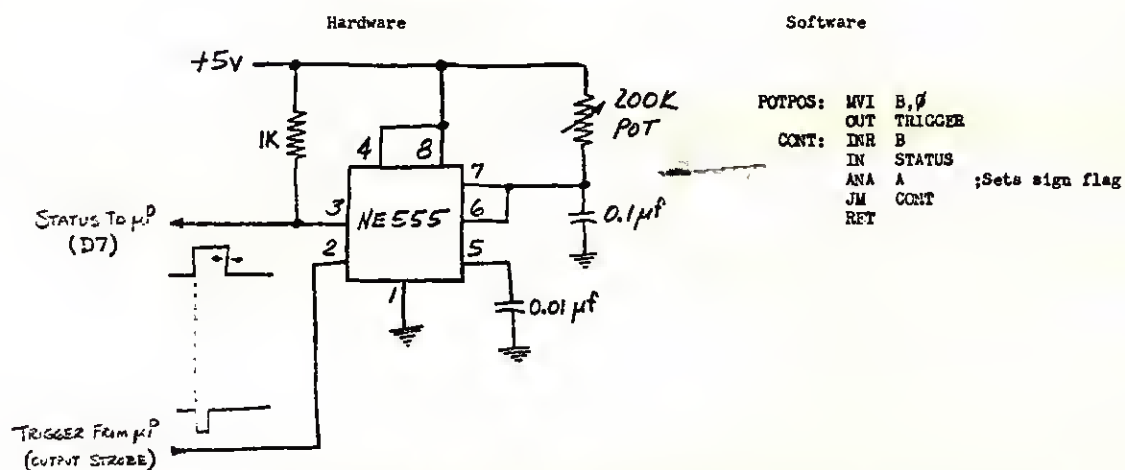

- NOTES:
1. Software written as a subroutine for the 8008/8080 microprocessors.
 2. The flags and registers A & B are affected by the subroutine.
 3. Register B contains the pot position on exit.

HOMEBREW COMPUTER CLUB NEWSLETTER
Post Office Box 626
Mountain View, CA 94042



FIRST CLASS MAIL

LENNY SHUSTER
P.O. BOX 3210
STANFORD, CA.

94088